

SI UNITS USED



# **ELECTRICAL CIRCUIT**

## **THEORY AND TECHNOLOGY**

**JOHN BIRD**  
**FIFTH EDITION**



Ref  
G21.3192  
B618  
2014  
7

3495

# 27891



# Electrical Circuit Theory and Technology

Fifth Edition  
by E. A. Preece  
London: Butterworths, 1963

Routledge  
Taylor & Francis Group

# Contents

Preface	xi	4.5 E.m.f. and internal resistance of a cell	29
<b>Part 1 Basic electrical engineering principles</b>	<b>1</b>	4.6 Primary cells	31
<b>1 Units associated with basic electrical quantities</b>	<b>3</b>	4.7 Secondary cells	32
1.1 SI units	3	4.8 Cell capacity	33
1.2 Charge	4	4.9 Safe disposal of batteries	35
1.3 Force	4	4.10 Fuel cells	35
1.4 Work	4	4.11 Alternative and renewable energy sources	35
1.5 Power	5		
1.6 Electrical potential and e.m.f.	6	<b>Revision Test 1</b>	<b>37</b>
1.7 Resistance and conductance	6	<b>5 Series and parallel networks</b>	<b>38</b>
1.8 Electrical power and energy	6	5.1 Series circuits	39
1.9 Summary of terms, units and their symbols	7	5.2 Potential divider	40
		5.3 Parallel networks	42
<b>2 An introduction to electric circuits</b>	<b>8</b>	5.4 Current division	44
2.1 Standard symbols for electrical components	9	5.5 Loading effect	47
2.2 Electric current and quantity of electricity	9	5.6 Potentiometers and rheostats	48
2.3 Potential difference and resistance	10	5.7 Relative and absolute voltages	51
2.4 Basic electrical measuring instruments	10	5.8 Earth potential and short circuits	52
2.5 Linear and non-linear devices	11	5.9 Wiring lamps in series and in parallel	52
2.6 Ohm's law	11		
2.7 Multiples and sub-multiples	11	<b>6 Capacitors and capacitance</b>	<b>54</b>
2.8 Conductors and insulators	13	6.1 Introduction to capacitors	55
2.9 Electrical power and energy	13	6.2 Electrostatic field	55
2.10 Main effects of electric current	16	6.3 Electric field strength	56
2.11 Fuses	16	6.4 Capacitance	56
2.12 Insulation and the dangers of constant high current flow	17	6.5 Capacitors	56
		6.6 Electric flux density	57
<b>3 Resistance variation</b>	<b>18</b>	6.7 Permittivity	57
3.1 Resistor construction	19	6.8 The parallel plate capacitor	59
3.2 Resistance and resistivity	19	6.9 Capacitors connected in parallel and series	60
3.3 Temperature coefficient of resistance	21	6.10 Dielectric strength	64
3.4 Resistor colour coding and ohmic values	23	6.11 Energy stored	65
		6.12 Practical types of capacitor	65
<b>4 Batteries and alternative sources of energy</b>	<b>26</b>	6.13 Supercapacitors	67
4.1 Introduction to batteries	27	6.14 Discharging capacitors	68
4.2 Some chemical effects of electricity	27		
4.3 The simple cell	28	<b>7 Magnetic circuits</b>	<b>69</b>
4.4 Corrosion	29	7.1 Introduction to magnetism and magnetic circuits	70
		7.2 Magnetic fields	70
		7.3 Magnetic flux and flux density	71
		7.4 Magnetomotive force and magnetic field strength	71
		7.5 Permeability and $B$ - $H$ curves	72
		7.6 Reluctance	73



7.7	Composite series magnetic circuits	75		
7.8	Comparison between electrical and magnetic quantities	78		
7.9	Hysteresis and hysteresis loss	78		
<b>Revision Test 2</b>		<b>80</b>		
<b>8</b>	<b>Electromagnetism</b>	<b>81</b>		
8.1	Magnetic field due to an electric current	82		
8.2	Electromagnets	83		
8.3	Force on a current-carrying conductor	85		
8.4	Principle of operation of a simple d.c. motor	88		
8.5	Principle of operation of a moving-coil instrument	89		
8.6	Force on a charge	89		
<b>9</b>	<b>Electromagnetic induction</b>	<b>91</b>		
9.1	Introduction to electromagnetic induction	92		
9.2	Laws of electromagnetic induction	92		
9.3	Rotation of a loop in a magnetic field	95		
9.4	Inductance	96		
9.5	Inductors	97		
9.6	Energy stored	98		
9.7	Inductance of a coil	99		
9.8	Mutual inductance	100		
<b>10</b>	<b>Electrical measuring instruments and measurements</b>	<b>103</b>		
10.1	Introduction	104		
10.2	Analogue instruments	104		
10.3	Moving-iron instrument	104		
10.4	The moving-coil rectifier instrument	105		
10.5	Comparison of moving-coil, moving-iron and moving-coil rectifier instruments	105		
10.6	Shunts and multipliers	106		
10.7	Electronic instruments	107		
10.8	The ohmmeter	108		
10.9	Multimeters	108		
10.10	Wattmeters	108		
10.11	Instrument 'loading' effect	109		
10.12	The oscilloscope	111		
10.13	Virtual test and measuring instruments	116		
10.14	Virtual digital storage oscilloscopes	116		
10.15	Waveform harmonics	120		
10.16	Logarithmic ratios	120		
10.17	Null method of measurement	123		
10.18	Wheatstone bridge	123		
10.19	D.c. potentiometer	123		
10.20	A.c. bridges	124		
10.21	Measurement errors	125		
<b>11</b>	<b>Semiconductor diodes</b>	<b>128</b>		
11.1	Types of material	129		
11.2	Semiconductor materials	129		
11.3	Conduction in semiconductor materials	131		
11.4	The p-n junction	131		
11.5	Forward and reverse bias	132		
11.6	Semiconductor diodes	135		
11.7	Characteristics and maximum ratings	136		
11.8	Rectification	136		
11.9	Zener diodes	136		
11.10	Silicon controlled rectifiers	138		
11.11	Light emitting diodes	138		
11.12	Varactor diodes	139		
11.13	Schottky diodes	139		
<b>12</b>	<b>Transistors</b>	<b>141</b>		
12.1	Transistor classification	142		
12.2	Bipolar junction transistors (BJTs)	142		
12.3	Transistor action	143		
12.4	Leakage current	144		
12.5	Bias and current flow	145		
12.6	Transistor operating configurations	145		
12.7	Bipolar transistor characteristics	145		
12.8	Transistor parameters	147		
12.9	Current gain	148		
12.10	Typical BJT characteristics and maximum ratings	149		
12.11	Field effect transistors	150		
12.12	Field effect transistor characteristics	150		
12.13	Typical FET characteristics and maximum ratings	152		
12.14	Transistor amplifiers	152		
12.15	Load lines	155		
<b>Revision Test 3</b>		<b>159</b>		
<b>Main formulae for Part 1 Basic electrical and electronic principles</b>		<b>161</b>		
<b>Part 2 Electrical principles and technology</b>		<b>163</b>		
<b>13</b>	<b>D.c. circuit theory</b>	<b>165</b>		
13.1	Introduction	165		
13.2	Kirchhoff's laws	166		
13.3	The superposition theorem	169		
13.4	General d.c. circuit theory	172		
13.5	Thévenin's theorem	174		
13.6	Constant-current source	178		
13.7	Norton's theorem	178		
13.8	Thévenin and Norton equivalent networks	181		
13.9	Maximum power transfer theorem	184		

<b>14 Alternating voltages and currents</b>	<b>187</b>		
14.1 Introduction	188	18.3 Op amp inverting amplifier	256
14.2 The a.c. generator	188	18.4 Op amp non-inverting amplifier	258
14.3 Waveforms	189	18.5 Op amp voltage-follower	259
14.4 A.c. values	190	18.6 Op amp summing amplifier	259
14.5 Electrical safety – insulation and fuses	193	18.7 Op amp voltage comparator	260
14.6 The equation of a sinusoidal waveform	193	18.8 Op amp integrator	261
14.7 Combination of waveforms	196	18.9 Op amp differential amplifier	262
14.8 Rectification	199	18.10 Digital to analogue (D/A) conversion	264
14.9 Smoothing of the rectified output waveform	200	18.11 Analogue to digital (A/D) conversion	264
<b>Revision Test 4</b>	<b>202</b>		
<b>15 Single-phase series a.c. circuits</b>	<b>203</b>	<b>Revision Test 5</b>	<b>266</b>
15.1 Purely resistive a.c. circuit	204	<b>19 Three-phase systems</b>	<b>267</b>
15.2 Purely inductive a.c. circuit	204	19.1 Introduction	268
15.3 Purely capacitive a.c. circuit	205	19.2 Three-phase supply	268
15.4 $R$ – $L$ series a.c. circuit	206	19.3 Star connection	268
15.5 $R$ – $C$ series a.c. circuit	209	19.4 Delta connection	271
15.6 $R$ – $L$ – $C$ series a.c. circuit	211	19.5 Power in three-phase systems	273
15.7 Series resonance	214	19.6 Measurement of power in three-phase systems	274
15.8 Q-factor	215	19.7 Comparison of star and delta connections	279
15.9 Bandwidth and selectivity	217	19.8 Advantages of three-phase systems	279
15.10 Power in a.c. circuits	217	<b>20 Transformers</b>	<b>280</b>
15.11 Power triangle and power factor	219	20.1 Introduction	281
<b>16 Single-phase parallel a.c. circuits</b>	<b>221</b>	20.2 Transformer principle of operation	281
16.1 Introduction	222	20.3 Transformer no-load phasor diagram	283
16.2 $R$ – $L$ parallel a.c. circuit	222	20.4 E.m.f. equation of a transformer	285
16.3 $R$ – $C$ parallel a.c. circuit	223	20.5 Transformer on-load phasor diagram	287
16.4 $L$ – $C$ parallel a.c. circuit	224	20.6 Transformer construction	288
16.5 $LR$ – $C$ parallel a.c. circuit	226	20.7 Equivalent circuit of a transformer	288
16.6 Parallel resonance and Q-factor	229	20.8 Regulation of a transformer	290
16.7 Power factor improvement	233	20.9 Transformer losses and efficiency	291
<b>17 D.c. transients</b>	<b>238</b>	20.10 Resistance matching	293
17.1 Introduction	239	20.11 Auto transformers	296
17.2 Charging a capacitor	239	20.12 Isolating transformers	298
17.3 Time constant for a $C$ – $R$ circuit	240	20.13 Three-phase transformers	298
17.4 Transient curves for a $C$ – $R$ circuit	240	20.14 Current transformers	299
17.5 Discharging a capacitor	244	20.15 Voltage transformers	300
17.6 Camera flash	246	<b>Revision Test 6</b>	<b>301</b>
17.7 Current growth in an $L$ – $R$ circuit	246	<b>21 D.c. machines</b>	<b>302</b>
17.8 Time constant for an $L$ – $R$ circuit	247	21.1 Introduction	303
17.9 Transient curves for an $L$ – $R$ circuit	247	21.2 The action of a commutator	303
17.10 Current decay in an $L$ – $R$ circuit	249	21.3 D.c. machine construction	304
17.11 Switching inductive circuits	251	21.4 Shunt, series and compound windings	304
17.12 The effect of time constant on a rectangular waveform	251	21.5 E.m.f. generated in an armature winding	305
<b>18 Operational amplifiers</b>	<b>253</b>	21.6 D.c. generators	306
18.1 Introduction to operational amplifiers	254	21.7 Types of d.c. generator and their characteristics	307
18.2 Some op amp parameters	255		



21.8	D.c. machine losses	311
21.9	Efficiency of a d.c. generator	311
21.10	D.c. motors	312
21.11	Torque of a d.c. machine	313
21.12	Types of d.c. motor and their characteristics	314
21.13	The efficiency of a d.c. motor	318
21.14	D.c. motor starter	320
21.15	Speed control of d.c. motors	321
21.16	Motor cooling	323
<b>22</b>	<b>Three-phase induction motors</b>	<b>324</b>
22.1	Introduction	325
22.2	Production of a rotating magnetic field	325
22.3	Synchronous speed	327
22.4	Construction of a three-phase induction motor	328
22.5	Principle of operation of a three-phase induction motor	328
22.6	Slip	329
22.7	Rotor e.m.f. and frequency	330
22.8	Rotor impedance and current	331
22.9	Rotor copper loss	331
22.10	Induction motor losses and efficiency	332
22.11	Torque equation for an induction motor	333
22.12	Induction motor torque–speed characteristics	335
22.13	Starting methods for induction motors	336
22.14	Advantages of squirrel-cage induction motors	337
22.15	Advantages of wound rotor induction motor	338
22.16	Double cage induction motor	338
22.17	Uses of three-phase induction motors	338
<b>Revision Test 7</b>		<b>339</b>
<b>Main formulae for Part 2 Electrical principles and technology</b>		<b>340</b>
<b>Part 3 Advanced circuit theory and technology</b>		<b>343</b>
<b>23</b>	<b>Revision of complex numbers</b>	<b>345</b>
23.1	Introduction	345
23.2	Operations involving Cartesian complex numbers	347
23.3	Complex equations	349
23.4	The polar form of a complex number	349
23.5	Multiplication and division using complex numbers in polar form	350
23.6	De Moivre's theorem – powers and roots of complex numbers	352
<b>24</b>	<b>Application of complex numbers to series a.c. circuits</b>	<b>354</b>
24.1	Introduction	354
24.2	Series a.c. circuits	355
24.3	Further worked problems on series a.c. circuits	361
<b>25</b>	<b>Application of complex numbers to parallel a.c. networks</b>	<b>366</b>
25.1	Introduction	366
25.2	Admittance, conductance and susceptance	367
25.3	Parallel a.c. networks	370
25.4	Further worked problems on parallel a.c. networks	374
<b>26</b>	<b>Power in a.c. circuits</b>	<b>377</b>
26.1	Introduction	377
26.2	Determination of power in a.c. circuits	378
26.3	Power triangle and power factor	380
26.4	Use of complex numbers for determination of power	381
26.5	Power factor improvement	385
<b>Revision Test 8</b>		<b>390</b>
<b>27</b>	<b>A.c. bridges</b>	<b>391</b>
27.1	Introduction	391
27.2	Balance conditions for an a.c. bridge	391
27.3	Types of a.c. bridge circuit	393
27.4	Worked problems on a.c. bridges	397
<b>28</b>	<b>Series resonance and Q-factor</b>	<b>401</b>
28.1	Introduction	402
28.2	Series resonance	402
28.3	Q-factor	404
28.4	Voltage magnification	406
28.5	Q-factors in series	408
28.6	Bandwidth	409
28.7	Small deviations from the resonant frequency	413
<b>29</b>	<b>Parallel resonance and Q-factor</b>	<b>416</b>
29.1	Introduction	416
29.2	The $LR-C$ parallel network	417
29.3	Dynamic resistance	418
29.4	The $LR-CR$ parallel network	418
29.5	Q-factor in a parallel network	419
29.6	Further worked problems on parallel resonance and Q-factor	423
<b>Revision Test 9</b>		<b>426</b>

<b>30 Introduction to network analysis</b>	<b>427</b>		
30.1 Introduction	427		
30.2 Solution of simultaneous equations using determinants	428		
30.3 Network analysis using Kirchhoff's laws	429		
<b>31 Mesh-current and nodal analysis</b>	<b>437</b>		
31.1 Mesh-current analysis	437		
31.2 Nodal analysis	441		
<b>32 The superposition theorem</b>	<b>448</b>		
32.1 Introduction	448		
32.2 Using the superposition theorem	448		
32.3 Further worked problems on the superposition theorem	453		
<b>33 Thévenin's and Norton's theorems</b>	<b>458</b>		
33.1 Introduction	458		
33.2 Thévenin's theorem	459		
33.3 Further worked problems on Thévenin's theorem	465		
33.4 Norton's theorem	469		
33.5 Thévenin and Norton equivalent networks	476		
<b>Revision Test 10</b>	<b>481</b>		
<b>34 Delta-star and star-delta transformations</b>	<b>482</b>		
34.1 Introduction	482		
34.2 Delta and star connections	482		
34.3 Delta-star transformation	483		
34.4 Star-delta transformation	491		
<b>35 Maximum power transfer theorems and impedance matching</b>	<b>495</b>		
35.1 Maximum power transfer theorems	496		
35.2 Impedance matching	501		
<b>Revision Test 11</b>	<b>504</b>		
<b>36 Complex waveforms</b>	<b>505</b>		
36.1 Introduction	506		
36.2 The general equation for a complex waveform	506		
36.3 Harmonic synthesis	507		
36.4 Fourier series of periodic and non-periodic functions	514		
36.5 Even and odd functions and Fourier series over any range	519		
36.6 R.m.s. value, mean value and the form factor of a complex wave	523		
36.7 Power associated with complex waves	526		
36.8 Harmonics in single-phase circuits	528		
36.9 Further worked problems on harmonics in single-phase circuits	532		
36.10 Resonance due to harmonics	536		
36.11 Sources of harmonics	538		
<b>37 A numerical method of harmonic analysis</b>	<b>542</b>		
37.1 Introduction	542		
37.2 Harmonic analysis on data given in tabular or graphical form	542		
37.3 Complex waveform considerations	546		
<b>38 Magnetic materials</b>	<b>549</b>		
38.1 Revision of terms and units used with magnetic circuits	550		
38.2 Magnetic properties of materials	550		
38.3 Hysteresis and hysteresis loss	552		
38.4 Eddy current loss	556		
38.5 Separation of hysteresis and eddy current losses	559		
38.6 Non-permanent magnetic materials	561		
38.7 Permanent magnetic materials	562		
<b>Revision Test 12</b>	<b>563</b>		
<b>39 Dielectrics and dielectric loss</b>	<b>564</b>		
39.1 Electric fields, capacitance and permittivity	564		
39.2 Polarization	565		
39.3 Dielectric strength	565		
39.4 Thermal effects	566		
39.5 Mechanical properties	567		
39.6 Types of practical capacitor	567		
39.7 Liquid dielectrics and gas insulation	567		
39.8 Dielectric loss and loss angle	567		
<b>40 Field theory</b>	<b>571</b>		
40.1 Field plotting by curvilinear squares	572		
40.2 Capacitance between concentric cylinders	575		
40.3 Capacitance of an isolated twin line	580		
40.4 Energy stored in an electric field	583		
40.5 Induced e.m.f. and inductance	585		
40.6 Inductance of a concentric cylinder (or coaxial cable)	585		
40.7 Inductance of an isolated twin line	588		
40.8 Energy stored in an electromagnetic field	590		
<b>41 Attenuators</b>	<b>593</b>		
41.1 Introduction	594		
41.2 Characteristic impedance	594		
41.3 Logarithmic ratios	596		
41.4 Symmetrical T- and $\pi$ -attenuators	598		
41.5 Insertion loss	603		
41.6 Asymmetrical T- and $\pi$ -sections	606		



## X Contents

41.7	The L-section attenuator	609	45.3	Response of $R$ - $L$ series circuit to a step input	696
41.8	Two-port networks in cascade	611	45.4	$L$ - $R$ - $C$ series circuit response	699
41.9	$ABCD$ parameters	614	45.5	Introduction to Laplace transforms	702
41.10	$ABCD$ parameters for networks	617	45.6	Inverse Laplace transforms and the solution of differential equations	706
41.11	Characteristic impedance in terms of $ABCD$ parameters	623	45.7	Laplace transform analysis directly from the circuit diagram	712
<b>Revision Test 13</b>		<b>625</b>	45.8	$L$ - $R$ - $C$ series circuit using Laplace transforms	721
<b>42 Filter networks</b>		<b>626</b>	45.9	Initial conditions	724
42.1	Introduction	626	<b>Revision Test 14</b>		<b>728</b>
42.2	Basic types of filter sections	627	<b>Main formulae for Part 3 Advanced circuit theory and technology</b>		<b>729</b>
42.3	The characteristic impedance and the attenuation of filter sections	629	<b>Part 4 General reference</b>		<b>735</b>
42.4	Ladder networks	630	Standard electrical quantities – their symbols and units		737
42.5	Low-pass filter sections	631	Greek alphabet		740
42.6	High-pass filter sections	637	Common prefixes		741
42.7	Propagation coefficient and time delay in filter sections	642	Resistor colour coding and ohmic values		742
42.8	' $m$ -derived' filter sections	648	Answers to Practice Exercises		743
42.9	Practical composite filters	653	Index		763
<b>43 Magnetically coupled circuits</b>		<b>656</b>	<b>On the Website</b>		
43.1	Introduction	656	<b>Some practical laboratory experiments</b>		
43.2	Self-inductance	656	1	Ohm's law	2
43.3	Mutual inductance	657	2	Series-parallel d.c. circuit	3
43.4	Coupling coefficient	658	3	Superposition theorem	4
43.5	Coils connected in series	659	4	Thévenin's theorem	6
43.6	Coupled circuits	662	5	Use of a CRO to measure voltage, frequency and phase	8
43.7	Dot rule for coupled circuits	667	6	Use of a CRO with a bridge rectifier circuit	9
<b>44 Transmission lines</b>		<b>674</b>	7	Measurement of the inductance of a coil	10
44.1	Introduction	674	8	Series a.c. circuit and resonance	11
44.2	Transmission line primary constants	675	9	Parallel a.c. circuit and resonance	13
44.3	Phase delay, wavelength and velocity of propagation	676	10	Charging and discharging a capacitor	15
44.4	Current and voltage relationships	677	To download and edit go to: <a href="http://www.routledge.com/cw/bird">www.routledge.com/cw/bird</a>		
44.5	Characteristic impedance and propagation coefficient in terms of the primary constants	679			
44.6	Distortion on transmission lines	683			
44.7	Wave reflection and the reflection coefficient	685			
44.8	Standing-waves and the standing-wave ratio	688			
<b>45 Transients and Laplace transforms</b>		<b>693</b>			
45.1	Introduction	694			
45.2	Response of $R$ - $C$ series circuit to a step input	694			



# Index

- ABCD networks in cascade, 615
  - parameters, 614
  - for networks, 617
- Absolute permeability, 72, 550
  - permittivity, 57, 58
  - voltage, 51
- A.c. bridges, 124, 391
  - generator, 188, 538
  - values, 190
- Acceptor circuit, 214
- Active networks, 627
  - power, 219, 380, 387, 527
- Admittance, 367
- Air capacitor, 65
- Alkaline cell, 27
- Alternating current, 187
  - waveforms, 189
- Alternative energy sources, 35
- Aluminium, 130
- Ammeter, 10, 106
- Ampere, 4, 9
- Amplifier gain, 256, 258
- Amplitude, 112, 190
- Analogue instrument, 104
- Analogue-to-digital conversion, 113, 264
- Anderson bridge, 487
- Angular velocity, 194
- Anode, 27, 136
- Antimony, 130
- Antinode, 689
- Apparent power, 219, 380
- Applications of resonance, 230
- Argand diagram, 345
- Argument, 350
- Armature, 304
  - reaction, 305
- Arsenic, 130
- Asymmetrical  $\pi$ -section, 606
  - T-section, 595, 606
- Atom, 9, 551
- Attenuation, 594, 597
  - bands, 626
  - coefficient, 643, 684
  - constant, 643, 678
- Attenuators, 593
  - asymmetrical  $\pi$ , 606
  - asymmetrical T, 594, 606
  - cascade, 611
  - L-section, 609
  - symmetrical  $\pi$ , 599
  - symmetrical T, 594, 598
- Attraction type of m.i. instrument, 104
- Audio-frequency transformer, 288
- Auto transformer, 296
  - starting, 337
- Auxiliary equations, 700
- Avalanche effect, 134
  - breakdown, 136
- Average value, 190
- Avometer, 10
- Back e.m.f., 312
- Band-pass filter, 628, 641
  - stop filter, 628
- Bandwidth, 217, 255, 409
- Barrier potential, 132
- Base, 144
- Batteries, 26, 27, 30
  - disposal of, 33
- Bell, electric, 16, 83
- B-H curves, 72, 552
- Bias, 145
- Bipolar junction transistor, 142, 145
  - characteristics, 145, 149
- Boron, 130
- Breakdown voltage, 134
- Bridge, a.c., 124, 391
- Bridge megger, 10, 108
  - rectifier, 136, 200
- Brush contact loss, 311
- Brushes, 303
- Buffer amplifier, 259
- Calibration accuracy, 125
- Camera flash, 246
- Candela, 4
- Capacitance, 56, 564, 675
  - between concentric cylinders, 575
  - of isolated twin line, 580
- Capacitive reactance, 205, 355
- Capacitors, 55, 56
  - charging, 239
  - discharging, 68, 244
  - energy stored in, 65
  - in parallel, 60
  - in series, 61
  - parallel plate, 59
  - practical types, 65, 567
  - reservoir, 201
- Carbon resistors, 19
- Car ignition, 16
- Cartesian complex numbers, 345
- Cathode, 27, 136
- Cell, 28, 31, 33
  - capacity, 33
- Ceramic capacitor, 66
- Characteristic impedance, 594, 623
  - in terms of ABCD parameters, 623
  - in terms of primary line constants, 679
  - of filters, 629
  - of transmission lines, 679
- Characteristics, d.c. generator, 306–311
  - d.c. machines, 305
  - d.c. motor, 312–318
  - of semiconductors, 136
  - of transistor, 145, 152
- Charge, 4, 57
  - density, 57
- Charged particles, 27
- Charging of cell, 30, 31
  - capacitor, 239, 694
- Chemical effect of electric current, 16
  - electricity, 27
- Choke, 98
- Circuit magnification factor, 406
  - theory, 172
- CIVIL, 206
- Class A amplifier, 154
- Closed-loop gain, 257
- Coaxial cable, 575
- Coefficient of coupling, 658
- Coercive force, 78, 552
- Cofactor, 429
- Coils in series, cumulatively coupled, 659
  - differentially coupled, 659
- Collector, 145
- Combination of waveforms, 196
- Commercial bridge, 125
- Common-mode rejection ratio, 255
- Commutation, 303
- Commutator, 303, 304
- Complex conjugate, 347
  - equations, 349

- Complex numbers, 345
  - applications to parallel networks, 366
  - applications to series circuits, 354
  - Cartesian form, 345
  - De Moivre's theorem, 352
  - determination of power, 381
  - equations, 349
  - operations involving, 347
  - polar form, 349
- Complex wave, 120, 506
  - form factor, 525
  - frequency, 713
  - general equation, 506
  - harmonics in single-phase circuits, 528
  - mean value, 525
  - power associated with, 526
  - resonance due to harmonics, 536
  - r.m.s. value, 523
  - sources of harmonics, 538
  - waveform considerations, 546
  - waveforms, 505
- Composite filters, 653
  - series magnetic circuits, 75
- Compound motor, 318
  - winding, 304
  - wound generator, 309
- Concentric cable, 575, 585
  - field plotting, 578
- Conductance, 6, 367, 675
- Conductor, 9, 13, 129
- Constant-current source, 178
- Constant-k high-pass filter, 640
  - low-pass filter, 634
- Contact potential, 131, 132
- Continuity tester, 11, 108
- Continuous function, 515
  - loading, 684
- Cooker, 16
- Copper loss, 291, 311
- Core loss, 311
  - component, 284
- Core type transformer construction, 288
- Corrosion, 29
- Coulomb, 4, 9, 57
- Coulomb's law, 56
- Coupled circuits, 662
  - dot rule, 667
- Coupling coefficient, 658
- Covalent bonds, 130
- Critically damped circuit, 700, 723
- Cumulative compound motor, 318
- Curie temperature, 552
- Current, 4, 9
  - decay in L-R circuit, 249, 698
  - division, 44, 370
  - gain, 148
  - growth in L-R circuit, 246, 696
  - magnification, 230, 419
  - main effects of, 16
  - transformer, 299
- Current gain in transistors, 148
- Curvilinear squares, 572
- Cut-off frequency, 627, 631
- Cycle, 189
  
- Damping, 89, 104, 722
  - device, 104
- D.c. circuit theory, 165, 172
  - generators, 396
  - machine construction, 304
  - machine losses, 311
  - machines, 302
  - motors, 89, 303, 312
  - motor starter, 320
  - potentiometer, 123
  - transients, 238
- Decibel, 120, 596
  - meter, 121
- Delta connection, 271, 482
- Delta-star comparison, 279
  - transformation, 483
- De Moivre's theorem, 352
- Depletion layer, 131, 132
- Derived units, 3
- De Sauty bridge, 125, 395
- Design impedance, 632
- Detector types, a.c. bridges, 392
- Determinants, 428
- Deviation from resonant frequency, 413
- Diamagnetism, 551
- Dielectric, 56, 58, 564
  - hysteresis, 567
  - liquid, 567
  - loss, 567
  - strength, 64, 565
  - stress, 576
- Differential amplifier, 261, 262
  - compound motor, 318
  - equation solution, 709
  - voltage amplifier, 254
- Differentiator circuit, 252
- Diffusion, 132
- Digital multimeter, 108
  - oscilloscopes, 104, 111, 113
  - voltmeter, 107
- Digital-to-analogue conversion, 264
- Dimensions of most economical cable, 577
- Diode characteristics, 136
- Dirac function, 704
- Discharging of capacitors, 68, 244, 696
  - cells, 30, 32
- Disposal of batteries, 33
- Dissipation factor, 568
- Distortion on transmission line, 683
- Diverter, 322
- Domains, 552
- Doping, 130
- Dot rule for coupled circuits, 667
- Double beam oscilloscope, 112
  - cage induction motor, 338
  - layer capacitance, 67
- Drift, 9
- Dust core, 562
- Dynamic current gain, 147, 157
  - resistance, 229, 418
  
- Earth, 51
  - potential, 52
- Edison cell, 33
- Eddy current loss, 291, 556
- Effective value, 190
- Efficiency of d.c. generator, 311
  - d.c. motor, 319
  - induction motor, 332
  - transformer, 291
- Electrical energy, 6, 14
  - measuring instruments and measurements, 10, 103
  - potential, 6
  - power, 6, 13
  - quantities and units, 737
  - safety, 193
  - symbols, 9
- Electric bell, 16, 83
  - cell, 28
  - circuit, 8
  - current, 19
  - field strength, 56, 564
  - fire, 16
  - flux density, 57, 564
  - force, 55
  - potential, 6
- Electrochemical series, 28
- Electrodes, 27
- Electrolysis, 27
- Electrolyte, 27, 32
- Electrolytic capacitors, 67
- Electromagnetic induction, 91, 92
  - laws of, 92
- Electromagnetic wave, 675
- Electromagnetism, 81
- Electromagnets, 83
- Electromotive force, 6, 29
- Electron, 9, 27, 129
- Electronic instruments, 107
- Electroplating, 16, 28



- Electrostatic field, 55
- E.m.f., 6, 29  
equation of transformer, 285  
in armature winding, 305
- Emitter, 144
- Energy, 4  
associated with travelling wave, 686  
electrical, 6, 14  
stored in capacitor, 65  
stored in electric field, 583  
stored in electromagnetic field, 590  
stored in magnetic field of inductor, 98, 591
- Equipotential lines, 572
- Equivalent circuit, transformer, 288
- Errors, measurement, 125
- Exponential growth and decay curves, 239
- Even function, 519, 546
- Farad, 56
- Faraday's laws of electromagnetic induction, 92
- Ferrites, 79, 562
- Ferromagnetic-cored coils, 538  
materials, 73, 551
- Field effect transistor, 142, 140  
amplifiers, 152  
characteristics, 150, 152
- Field plotting, 572  
theory, 571
- Filter networks, 201, 626  
band-pass, 628  
band-stop, 628  
composite, 653  
high-pass, 627, 637  
low-pass, 627, 631  
'm derived', 648  
time delay, 646
- Final value theorem, 705
- Finite discontinuities, 515
- Fleming's left-hand rule, 86  
right-hand rule, 93
- Fluke, 10, 108
- Flux density, 71, 550  
electric, 57  
linkage, 585
- Flux, magnetic, 71, 550
- Force, 4  
on a charge, 89  
current-carrying conductor, 85
- Forced magnetization, 539  
resonant frequency, 419
- Form factor, 190, 525
- Formulae, 161, 340, 729
- Forward bias, 132  
characteristics, 133  
transconductance, 151
- Fourier coefficients, 515
- Fourier cosine series, 519
- Fourier series, 508, 514  
for non-periodic functions, 516  
for periodic functions, 514  
over any range, 521
- Fourier sine series, 520
- Free magnetization, 539
- Frequency, 112, 189, 194  
resonant, 214, 229
- Friction and windage losses, 311
- Fuel cell, 35
- Full wave rectification, 136, 200
- Fundamental, 120, 506, 515
- Furnace, 16
- Fuse, 16, 193
- Gallium arsenide, 130
- Galvanometer, 123
- Gas insulation, 567
- Generator, 16, 303, 306  
a.c., 188  
efficiency of, 311
- Geothermal energy, 36
- Germanium, 130, 134
- Gravitational force, 4
- Greek alphabet, 740
- Grip rule, 83
- Half-power points, 217, 409  
-wave rectification, 199  
-wave rectifier, 136, 199
- Harmonic analysis, 507  
numerical method, 508, 542
- Harmonic resonance, 536  
synthesis, 507, 508
- Harmonics, 120, 506, 515  
in single phase circuits, 528  
sources of, 538
- Hay bridge, 125, 394
- Heating effect of electric current, 16
- Heaviside bridge, 125
- Henry, 96, 585
- Hertz, 189
- High-pass filter, 627, 631, 637  
ladder, 631  
'm derived', 651
- Hole, 131
- Hydroelectricity, 36
- Hydrogen cell, 35
- Hysteresis, 78, 552  
loop, 78, 553  
loss, 78, 291, 553
- Image impedance, 606
- Imaginary numbers, 345
- Impedance, 206, 210  
matching, 501  
triangle, 206, 210
- Impulse, 703
- Impurity, 130
- Incident wave, 685
- Indium, 130
- Indium arsenide, 130
- Induced e.m.f., 88, 585
- Inductance, 96, 585, 675  
mutual, 96, 100  
of a coil, 99  
of a concentric cylinder, 585, 586  
of an isolated twin line, 588, 675
- Induction motor, three-phase, 324, 325  
construction, 328  
copper loss, 331  
double cage, 338  
impedance and current, 331  
losses and efficiency, 332  
principle of operation, 328  
production of rotating magnetic field, 325  
rotor e.m.f. and frequency, 330  
starting, 336  
torque equation, 333  
speed characteristic, 335  
uses, 338
- Inductive circuit, switching, 251  
reactance, 204, 355
- Inductors, 97
- Initial conditions, 724  
value theorem, 705
- Initial slope and three-point method, 240
- Input bias current, 255  
impedance, 257, 259, 629  
offset current, 255  
voltage, 255
- Insertion loss, 603  
ratio, 604
- Instantaneous values, 190
- Instrument 'loading' effect, 109
- Insulated gate field effect transistor (IGFET), 150
- Insulation, 193
- Insulation and dangers of high current, 17
- Insulation resistance tester, 11, 108
- Insulator, 9, 13, 129
- Integrated circuit, 139
- Integrator circuit, 251  
op amp, 261
- Internal resistance of a cell, 29
- Interpoles, 304

- Inverse Laplace transforms, 706
- Inverting op amp, 256
- Ion, 9, 27
- Iron, 16
  - loss, 291, 311
- Isolating transformer, 298
- Iterative impedance, 594, 606
  
- Joule, 4, 6, 14
- Junction gate field effect transistor (JFET), 150
  
- Kelvin, 4
- Kettle, 16
- kilo, 4
- Kilowatt-hour, 6, 14
- Kirchhoff's laws, a.c., 428, 429
  - d.c., 164
  - in the  $s$ -domain, 713
  - network analysis, a.c., 428
  
- Ladder networks, 631
- Lag, angle of, 193
- Lamps in series and parallel, 52
- Laplace transforms, 702
  - by partial fractions, 708
  - capacitor, 712
  - definition of, 702
  - elementary functions, 702
  - final value theorem, 705
  - inductor, 712
  - initial conditions, 724
  - initial value theorem, 705
  - inverse, 706
  - L-R-C circuit, 721
  - of derivatives, 705
  - resistor, 712
  - to solve differential equations, 709
- Lap winding, 304
- Laws of electromagnetic induction, 92
- L-C parallel network, 224
- Lead-acid cell, 32
- Lead, angle of, 193
- Leakage currents, 144, 567
- Leclanche cell, 32
- Lenz's law, 92
- Letter and digit code for resistors, 24
- Level compounded machine, 310
- Lifting magnet, 16, 84
- Light emitting diodes, 136, 138
- Linear device, 11
  - scale, 104
- Liquid dielectrics, 567
- Lithium-ion battery, 27
- Loading effect, 47, 109
- Load line, 155
  
- Local action, 28
- Logarithmic ratios, 120, 596
- Long shunt compound generator, 309
  - motor, 318
- Loop currents, 437
  - inductance, 589
- Loss angle, 567
- Losses in d.c. machines, 311
  - induction motor, 332
  - transformers, 291
- Loudspeaker, 85
- Low-pass filter, 627, 631, 635
  - ladder, 630
  - 'm derived', 650
- LR-C parallel network, 226
  - resonance, 417
- L-R-C circuit using Laplace transforms, 721
- LR-CR parallel network resonance, 418
- L-R-C series circuit, 699
- L-section attenuator, 609
- Luminous intensity, 4
- Lumped loading, 684
  
- Magnetically coupled circuits, 656
- Magnetic effect of electric current, 16
  - circuit, 69, 70
  - field, 70, 550
    - strength, 71, 550
  - flux, 70, 550
    - density, 70, 550
  - force, 70
  - materials, 549
  - moment, 551
  - properties of materials, 550
  - screens, 73
  - space constant, 72
- Magnetic field due to electric current, 82
- Magnetising component, 283
  - force, 71
- Magnetization curves, 72, 550
- Magnetomotive force, 71, 550
- Magnification factor, 406
- Majority carriers, 131, 132
- Manganese battery, 27
- Matched network, 604
- Matching transformer, 293, 501
- Maximum efficiency, transfer, 292
- Maximum power transfer theorems,
  - d.c., 184
  - a.c., 495, 496
- Maximum repetitive reverse voltage, 136
- Maximum value, 190
- Maxwell bridge, 125, 393
- Maxwell-Wien bridge, 395
  
- Maxwell's theorem, 438
- Mechanical analogy of parallel resonance, 230
- Mean value, 190
  - of complex wave, 525
- Measurement errors, 125
  - of power in three phase systems, 274
- 'm derived' filter, 648
- Mega, 4
- Megger, 11, 108
- Mercury cell, 32
- Mesh-connection, 271, 482
  - current analysis, 437
- Metal oxide resistors, 19
- Mica capacitor, 66
- Micro, 4
- Microelectronic systems, 541
- Milli, 4
- Minor, 429
- Minority carriers, 131
- Mismatched load, 685
- Modulus, 350
- Mole, 4
- Moore's circle technique, 573
- Motor, 16, 303, 312
  - compound, 318
  - cooling, 323
  - d.c., principle of operation, 88
  - efficiency, 318
  - speed control, 321
  - starter, 330
- Moving coil instrument, principle of, 89
  - rectifier instrument, 105
- Moving iron instrument, 104
- Multimeter, 108
- Multiples, 11
- Multiplier, 106
- Mutual inductance, 96, 100, 657
  
- Nano, 4
- National grid, 188
- Natural frequency, 419
- Negative feedback, 255
- Nepers, 596
- Network analysis, 427
- Neutral point, 268
- Neutron, 9
- Newton, 4, 85
- Nickel cadmium cells, 33
- Nickel-iron alloys, 562
- Nickel metal cells, 33
- Nife cell, 33
- Nodal analysis, 441
- Node, 441, 689
- No load phasor diagram, transformer, 283



- Nominal impedance, 632, 638  
 Non inverting amplifier, 258  
 Non-linear device, 11  
   scale, 104  
 Nonpermanent magnetic materials, 561  
 Norton and Thévenin equivalent networks, a.c., 476  
   d.c. 181  
 Norton's theorem, a.c., 469  
   d.c., 178  
 n-p-n transistor, 144  
 n-type material, 130  
 Nucleus, 9  
 Null method of measurement, 123  
 Numerical methods, 508  
   of harmonic analysis, 542  
 Nyquist, 117
- Odd functions, 520, 546  
 Ohm, 6, 10  
 Ohmic values, 23, 24, 742  
 Ohmmeter, 10, 108  
 Ohm's law, 11  
 On load phasor diagram, transformer, 287  
 Operating point, 156  
 Operational amplifiers, 253  
   differential, 262  
   integrator, 261  
   inverting amplifier, 256  
   non-inverting amplifier, 258  
   parameters, 255  
   summing amplifier, 259  
   voltage comparator, 260, 265  
   voltage follower, 259  
 Oscilloscope, analogue, 10, 111  
   digital, 111, 113  
   double beam, 114  
 Over-compounded machine, 310  
 Over-damped circuit, 700, 723  
 Owen bridge, 125, 394
- Paper capacitor, 66  
 Parallel networks, 42, 212, 366, 370  
   plate capacitor, 59  
   resonance, 229, 416  
 Paramagnetism, 551  
 Partial fractions, 708  
 Passbands, 626  
 Passive network, 627  
 Peak factor, 190  
 Peak inverse voltage, 136  
   value, 112, 190  
 Peak-to-peak value, 190  
 Pentavalent impurity, 130
- Period, 189, 506  
 Periodic function, 506, 515  
   time, 189, 194  
 Permanent magnet, 70, 562  
   magnetic materials, 562  
 Permeability, absolute, 72, 550  
   of free space, 72, 550  
   relative, 72, 550  
 Permeance, 550  
 Permittivity, 57  
   absolute, 58  
 Permittivity of free space, 58  
   relative, 58, 564  
 Phase delay, 676  
   shift coefficient, 643, 678, 684  
 Phasor, 193  
 Phosphorus, 130  
 Photovoltaic cells, 35  
 Pico, 4  
 $\pi$ -attenuator, 595, 599, 606  
 $\pi$ -connection, 482  
 $\pi$ -section m-derived filter, 649  
 Plastic capacitors, 67  
 p-n junction, 131  
 p-n-p transistor, 143  
 Polar form of complex number, 349  
 Polarization, 28, 565  
 Poles, 304  
 Potential difference, 6, 10  
   divider, 40  
   gradient, 56  
 Potentiometer, 40, 48, 123  
 Power, 5, 13  
   associated with complex waves, 526  
   factor, 219, 380, 527, 568  
   improvement, 233, 385  
   gain, 157  
   in a.c. circuits, 217, 222, 377  
   in three phase systems, 273  
   loss, 568  
   transformer, 288  
   triangle, 219, 380  
 Practical types of capacitor, 65  
 Prefixes, 4, 12, 741  
 Primary cell, 16, 27, 31  
   constants, 675  
 Principal node, 441  
 Principle of operation, d.c. motor, 88  
   m.c. instrument, 89  
   three-phase induction motor, 328  
   transformer, 281  
 Product-arm bridge, 393  
 Propagation coefficient, 642, 680  
   constant, 642, 678  
 Protons, 9, 129  
 Prototype filter, 635
- Pseudocapacitance, 67  
 p-type material, 130
- Q-factor, 215, 230, 404, 419  
   in series, 408  
 Quantity of electric charge, 9  
 Quiescent point, 155
- Radio frequency transformer, 288  
 Rating of a machine, 380  
   transformer, 282  
 Ratio-arm bridge, 393  
 R-C parallel network, 223  
   series circuit, 209, 357, 694  
 Reactive power, 219, 380  
 Real number, 345  
 Reciprocity theorem, 616  
 Rectangular complex number, 345  
 Rectification, 136, 199  
 Rectifier, 136, 538  
 Rectifier diode, 136  
 Reference level, 121  
 Reflected impedance, 664  
   wave, 685  
 Reflection coefficient, 686  
 Regulation of a transformer, 290  
 Rejector circuit, 230  
 Relative permeability, 72, 550  
   permittivity, 58, 564  
   voltage, 51  
 Relay, 16, 84  
 Reluctance, 73, 550  
 Remanence, 78, 552  
 Renewable energy sources, 35  
 Repulsion type of m.i. instrument, 105  
 Reservoir capacitor, 201  
 Residual flux density, 78, 552  
 Resistance, 6, 10, 19, 675  
   dynamic, 229  
   internal, 29  
   matching, 293  
   variation, 18  
 Resistivity, 19  
 Resistor colour coding, 23, 742  
   construction, 19  
 Resonance, applications of, 230  
 Resonance, by tuning capacitors, 665  
   due to harmonics, 536  
   parallel, 229, 416  
   series, 211, 214, 401, 402  
 Reverse bias, 132  
   characteristics, 133  
 Rheostat, 49  
 Ripple, 201  
 R-L-C circuit using Laplace transforms, 721

- R-L-C series circuit, 211, 357
- R-L parallel network, 222
  - series circuit, 206, 356, 696
- R.m.s. value, 112, 190
  - complex wave, 523
- Roots of auxiliary equation, 701
- Rotation of loop in magnetic field, 95
- Rotor copper loss, 331
  
- s-domains, 712
  - Kirchhoff's laws, 713
- Saturation flux density, 78, 552
- Schering bridge, 125, 396, 398
- Schottky diodes, 139
- Screw rule, 82, 83
- Secondary cell, 16, 27, 32
  - line constants, 678
- Selective resonance, 536
- Selectivity, 217, 411
- Self-excited generator, 306
- Self inductance, 96, 656
- Semiconductor diodes, 128, 135
  - materials, 129, 130
- Semiconductors, 128, 130
- Separately-excited generator, 306, 307
- Separation of hysteresis and eddy current losses, 559
- Series circuit, 39
  - a.c., 354, 355
- Series magnetic circuit, 75
  - resonance, 211, 214, 401, 402
  - winding, 304
  - wound motor, 316, 322
  - generator, 309
- Shells, 9, 129
- Shell type transformer construction, 288
- Short circuits, 52
- Short-shunt compound motor, 318
- Shunt, 106
  - field regulator, 321
  - winding, 304
  - wound generator, 308
  - motor, 314, 321
- Siemens, 6, 367
- Silicon, 130
- Silicon controlled rectifiers, 138
- Silicon-iron alloys, 561
- Silver oxide batteries, 27
- Simple cell, 28
- Simultaneous equations using determinants, 428
- Single-phase parallel a.c. network, 221
  - series a.c. circuit, 203
  - supply, 268
- Sine wave, 189
  - general equation, 193
- S.I. units, 3, 4
- Skin effect, 585
- Slew rate, 256
- Slip, 329
- Smoothing of rectified output, 200
- Solar energy, 35
- Soldering iron, 16
- Solenoid, 82
- Sources of harmonics, 538
- Spectrum analysis, 119
- Speed control of d.c. motors, 321
- Squirrel-cage induction motor, 336
  - applications of, 337
  - rotor, 328, 336
- Standing wave, 688, 689
  - ratio, 690
- Star connection, 268, 483
- Star-delta comparison, 279
  - starting, 337
  - transformation, 491
- Star point, 268
- Stator, 304
- Steady state, 239, 694
- Steinmetz index, 554
- Step input, L-R-C circuit, 721
  - R-C circuit, 694
  - R-L circuit, 696
- Stopbands, 626
- Streamline, 572
- Stroboscope, 11
- Sub-multiples, 11
- Summing amplifier, 250, 264
  - point, 260
- Supercapacitors, 67
  - applications of, 67
- Superposition theorem, a.c., 448
  - d.c., 169
- Surface mount technology, 19
- Susceptance, 367
- Switched-mode power supplies, 139
- Switching inductive circuits, 251
- Symmetrical lattice, 620
  - $\pi$ -attenuator, 599
  - T-attenuator, 594, 598
- Synchronous speed, 325, 327
  
- Tachometer, 11
- Tangent method, 240
- T-attenuator, 598
- T-connection, 483
- T-section m-derived filter, 648
- Telephone receiver, 84
- Temperature coefficient of resistance, 21
- Tesla, 71, 550
- Thermal effects of dielectrics, 566
- Thermodynamic temperature, 4
- Thévenin's theorem, a.c., 458
  - d.c., 174
- Thévenin and Norton equivalent networks, 181, 476
- Three-phase induction motors, 324, 325
  - construction, 328
  - copper loss, 331
  - double cage, 338
  - impedance and current, 331
  - losses and efficiency, 332
  - principle of operation, 328
  - production of rotating magnetic field, 325
  - rotor e.m.f. and frequency, 330
  - starting, 336
  - torque equation, 333
  - speed characteristics, 335
  - uses, 338
- Three-phase systems, 267
  - advantages of, 279
  - power, 273
  - transformers, 298
- Thyristor, 138, 540
- Tidal power, 36
- Time constant, C-R circuit, 240
  - L-R circuit, 247
- Time delay, 646
- Titanium oxide capacitor, 67
- Torque of a d.c. machine, 313
- Torque-speed characteristic of induction motor, 335
- Transfer characteristics, 146, 254
- Transformation ratio, 281
- Transformer, 16, 280
  - a.f., 288
  - auto, 296
  - cooling, 288
  - construction, 288
  - current, 299
  - e.m.f. equation, 285
  - equivalent circuit, 288
  - isolating, 298
  - losses and efficiency, 291
  - maximum efficiency, 292
  - no-load phasor diagram, 283
  - on-load phasor diagram, 287
  - power, 288
  - principle of operation, 281
  - rating, 282
  - regulation, 290
  - r.f., 288
  - three-phase, 298
  - voltage, 300
  - windings, 288



- Transient curves, C–R, 240, 694
  - L–R, 247, 696
- Transients, 239, 693
- Transistor, 141, 538
  - action, 143
  - amplifier, 143
  - characteristics, 145, 149
  - connections, 143
  - maximum ratings, 149
  - symbols, 143
- Transistor classification, 142
  - operating configurations, 142
  - parameters, 147
- Transit time, 646
- Transmission lines, 674
  - current and voltage relationships, 677
  - distortion, 683
  - primary constants, 675
  - secondary constants, 678
  - standing waves, 688
  - wave reflection, 685
- Transmission matrix, 615
  - parameters, 614
- Trapezoidal rule, 543
- Travelling wave, 675
- Trivalent impurity, 130
- True power, 219
- Two port networks, 594
  - in cascade, 611
- Types of a.c. bridge circuits, 393
  - capacitor, 65
  - material, 129
- UK supply voltage, 269
- Ultracapacitors, 67
- Under compounded machine, 310
- Underdamped circuit, 700, 722
- Unit of electricity, 14
- Units, 3, 7
  - S.I., 3, 4
- Universal bridge, 125
  - instrument, 108
- Vacuum, 57
- Valence electrons, 130
  - shell, 129
- Valves, 538
- Varactor diodes, 136, 139
- Variable air capacitor, 65
- Velocity of propagation, 677, 684
- Virtual digital storage oscilloscope, 116
  - earth, 256
  - test and measuring instruments, 116
- Volt, 6, 10
- Voltage, 9, 10
  - absolute, 51
  - comparator, 260, 265
  - follower op amp, 259
  - gain, 157
  - magnification at resonance, 215, 406
  - regulator, 137
  - relative, 51
  - transformer, 300
  - triangle, 206, 209
- Voltmeter, 10, 27, 106
- Water heater, 16
- Watt, 5, 13
- Wattmeter, 11, 108
- Waveform analyser, 508
  - considerations, 546
  - harmonics, 120
- Waveforms, 189
  - combination of, 196
- Wavelength, 676
- Wave reflection, 685
  - winding, 304
- Weber, 71, 550
- Weight, 4
- Wheatstone bridge, 123, 167, 391
- Wien bridge, 125, 396, 398
- Wind power, 36
- Wire wound resistors, 19
- Work, 4
- Wound rotor, 328, 337
  - induction motor, 336
  - advantages of, 338
- Yoke, 304
- Zener diode, 136
  - effect, 134