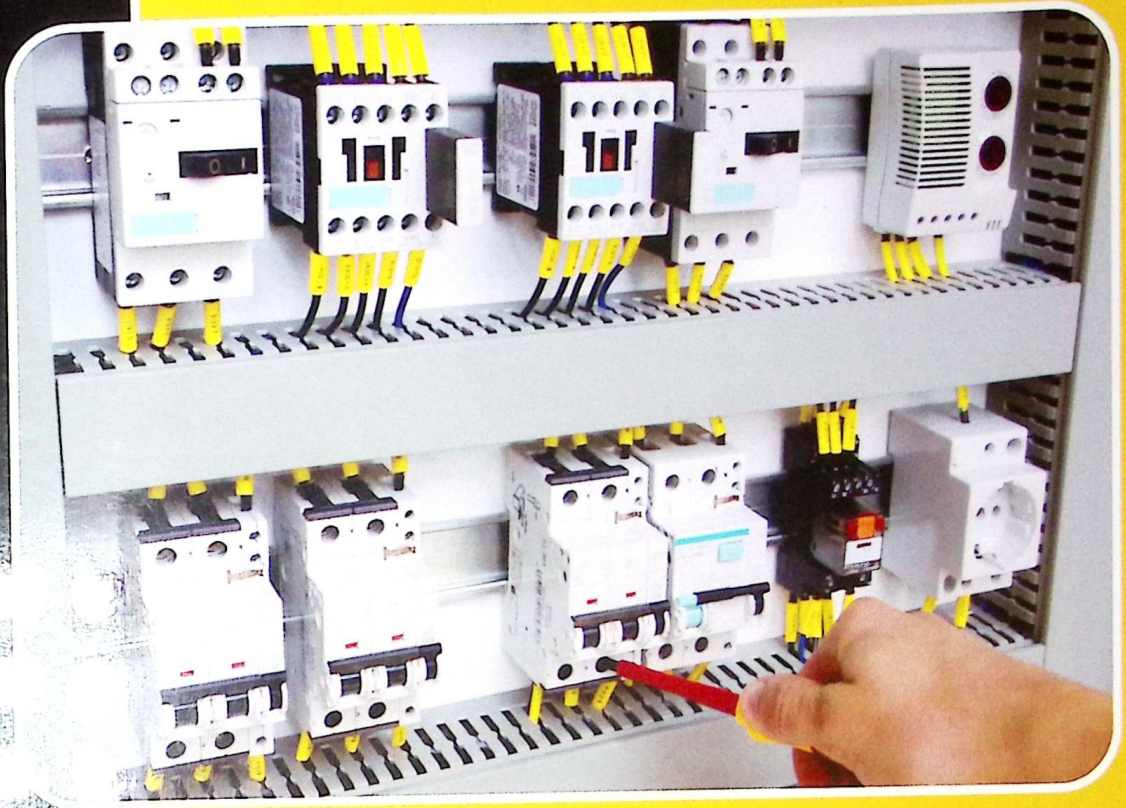


Textbook
Series



Electrical Engineering

Susan Curtis


 Larsen & Keller

Electrical Engineering

Susan Curtis

Electrical Engineering
Susan Curtis
ISBN: 978-1-64172-213-1 (Paperback)

© 2023 Larsen & Keller

 Larsen & Keller

Published by Larsen and Keller Education,
5 Penn Plaza,
19th Floor,
New York, NY 10001, USA

Cataloging-in-Publication Data

Electrical engineering / Susan Curtis.

p. cm.

Includes bibliographical references and index.

ISBN 978-1-64172-213-1

1. Electrical engineering. 2. Engineering. I. Curtis, Susan.

TK145 .E44 2023

621.3--dc23

This book contains information obtained from authentic and highly regarded sources. All chapters are published with permission under the Creative Commons Attribution Share Alike License or equivalent. A wide variety of references are listed. Permissions and sources are indicated; for detailed attributions, please refer to the permissions page. Reasonable efforts have been made to publish reliable data and information, but the authors, editors and publisher cannot assume any responsibility for the validity of all materials or the consequences of their use.

Trademark Notice: All trademarks used herein are the property of their respective owners. The use of any trademark in this text does not vest in the author or publisher any trademark ownership rights in such trademarks, nor does the use of such trademarks imply any affiliation with or endorsement of this book by such owners.

The publisher's policy is to use permanent paper from mills that operate a sustainable forestry policy. Furthermore, the publisher ensures that the text paper and cover boards used have met acceptable environmental accreditation standards.

Printed in the United States of America.

For more information regarding Larsen and Keller Education and its products, please visit the publisher's website www.larsen-keller.com

Table of Contents

Preface

VII

| | | |
|------------------|---|------------|
| Chapter 1 | What is Electrical Engineering? | 1 |
| a. | Electricity | 2 |
| b. | Electromagnetism | 5 |
| c. | Electric Current | 18 |
| d. | Electric Power | 19 |
| e. | Electrical Units | 21 |
| f. | Electrical Resistance | 25 |
| Chapter 2 | Subfields of Electrical Engineering | 28 |
| a. | Power Engineering | 28 |
| b. | Control Engineering | 32 |
| c. | Telecommunications Engineering | 35 |
| d. | Electronic Engineering | 45 |
| e. | Signal Processing | 47 |
| f. | Instrumentation | 50 |
| Chapter 3 | Electrical Circuits | 53 |
| a. | Series and Parallel Circuits | 54 |
| b. | AC Circuit | 61 |
| c. | DC Circuit | 63 |
| d. | RL Circuit | 66 |
| e. | RC Circuit | 74 |
| f. | RLC Circuit | 82 |
| g. | Wiring Diagram | 97 |
| h. | Electrical Circuit Breaker | 99 |
| Chapter 4 | Electrical Laws and Circuit Theorems | 118 |
| a. | Ohm's Law | 118 |
| b. | Ampère's Circuital Law | 121 |
| c. | Gauss's Law | 128 |

| | |
|---|-----|
| d. Coulomb's Law | 134 |
| e. Faraday's Law of Electromagnetic Induction | 144 |
| f. Lenz's Law | 154 |
| g. Circuit Theorems | 156 |
| h. Superposition Theorem | 160 |
| i. Thevenin's Theorem | 164 |
| j. Norton's Theorem | 167 |
| k. Maximum Power Transfer Theorem | 169 |

Tools and Instruments in Electrical Engineering **174**

| | |
|-----------------------|-----|
| a. LCR Meter | 174 |
| b. Voltmeter | 177 |
| c. Ohmmeter | 179 |
| d. Ammeter | 181 |
| e. Current Clamp | 185 |
| f. Multimeter | 188 |
| g. Network Analyzer | 203 |
| h. Megger | 208 |
| i. Power Factor Meter | 213 |
| j. Wattmeter | 218 |

Permissions

Index

Index

A

Ac Circuit, 14, 61-63, 108, 218
Active Power, 20-21, 218
Alternating Current, 1, 15, 18, 23, 61-62, 167, 175, 185, 190-191, 198, 220
Alternating Voltage, 62, 190
Analog Electronics, 45, 75
Angular Frequency, 67, 76, 83, 87
Apparent Power, 20-21, 25, 218
Arc Lamps, 28-29, 58
Attenuation, 39, 42, 44, 84-85, 87-88, 91, 96, 206

B

Bandwidth, 34, 39, 70, 78, 85, 91, 94-95, 179, 199

C

Capacitance, 23, 42, 44, 56, 59, 61-63, 74-75, 86, 91, 97, 174-175, 191, 193, 202, 207-208, 218, 223
Circuit Breaker, 98-117
Circuit Resistance, 21, 120-121
Complex Impedance, 67, 75
Computer-aided Design, 35, 44
Control Engineering, 28, 32-35, 46-47, 52
Control Theory, 32-34, 47
Coulomb Force, 7, 134, 137
Current Transformers, 99, 102, 106-107, 109
Cutoff Frequency, 70, 78

D

Demodulation, 46, 49
Dielectric Strength, 101, 115
Digital Signal Processors, 34, 48, 50
Diodes, 45, 193, 199
Dirac Delta Function, 69, 78, 133

E

Eddy Currents, 15, 154
Electric Field, 5, 8-9, 11-12, 15-17, 83, 123-124, 128-134, 137-138, 141, 145, 148-149, 154-155, 158, 221
Electric Forces, 5, 7, 9, 154
Electric Power, 3-5, 11-12, 14-15, 19-20, 28-30, 45, 62, 103, 106, 110, 181, 218

Electrical Circuits, 33-34, 53, 91, 118-119, 156, 160
Electrical Conductance, 55, 58
Electrical Energy, 3, 5, 11, 29-31, 188, 218, 220
Electromagnetic Induction, 28, 118, 144-146, 153, 212
Electromagnetic Waves, 6, 11, 17-18, 37, 40, 46, 124
Electromagnetism, 1, 5-8, 12, 17, 27, 121, 134, 136, 144, 149-150, 154-155, 173
Electromotive Force, 12, 14-15, 21, 144-148, 151, 154

F

Frequency Domain, 33-34, 48, 50, 70, 78, 92, 164
Frequency Modulation, 46

I

Imaginary Unit, 67, 76, 90
Impulse Response, 48, 66, 69-70, 78
Infinite Impulse Response, 48, 66
Instantaneous Value, 63, 205

L

Laplace Transform, 33, 35, 69, 71, 73, 78-79, 89
Law Of Resistance, 25

M

Magnetic Field, 1, 3, 5, 8-19, 56, 72, 83, 100-101, 104, 121, 123-125, 144-150, 152-156, 177, 181-182, 184-185, 187-189, 201, 211-212, 214, 216, 221, 223
Magnetic Flux, 12-15, 145-155, 185, 221
Magnetic Monopoles, 11, 17
Magnetization Current, 123, 126-127
Mutual Inductance, 13-14, 56, 58-59, 215, 223

N

Natural Response, 70, 75
Neutrons, 2, 4
Nuclear Power, 2, 4

O

Ohmmeter, 25-26, 174, 179-181, 191
Open Loop Control, 35
Optical Fiber, 35, 39-40, 46
Oscillator Circuits, 83, 96

P

Parallel Circuit, 53-54, 57-58, 64-66, 74, 82, 91-92, 96, 120

Passive Filters, 48, 66, 75

Power Consumption, 30, 46, 220-221

Power Engineering, 28-29, 45

Power Factor Meter, 174, 213-217

Power Grid, 29

Power Transmission, 28-29, 107, 185

Printed Circuit Boards, 45-46, 52

Q

Quantum Electrodynamics, 17, 139

R

Radio Frequency, 1, 200, 205, 218, 220

Radio Waves, 11, 40-41, 83

Real Power, 20-21, 25, 219

Resistance Units, 55, 57

S

Scaled Parameters, 85, 91

Series Circuit, 53-55, 61, 64, 68, 74, 76, 82, 86, 91-93, 95-96

Signal Processing, 1, 45-50, 186

Sinusoidal Steady State, 67, 76, 90

Solenoids, 50, 100, 144

Source Voltage, 54, 73, 197

T

Transfer Function, 68-69, 76-78, 82

Transmission Control Protocol, 38

Transmission Medium, 40

V

Volt-amperes, 25, 219

Voltage Divider, 68, 76, 164, 192, 194, 196

Voltage Drops, 54-55

Voltage Source, 62, 66, 72, 80, 86, 89, 91, 161-162, 164-167, 184, 201-202

W

Waveform, 49, 62-63, 89, 97, 100, 182, 185, 191, 196, 198, 220

Wiring Diagram, 97-98